

ECE 531
Microelectronics
Assignment 7

Aditya Sankaramanchi
101266059

Problem 1:

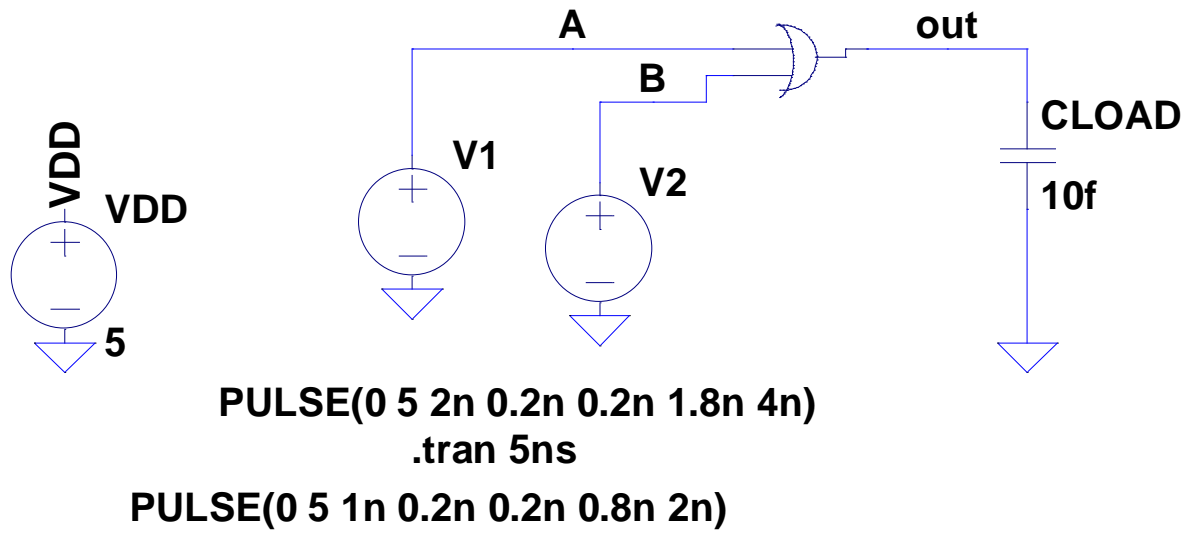


Figure 1: Test circuit to verify the operation of OR gate

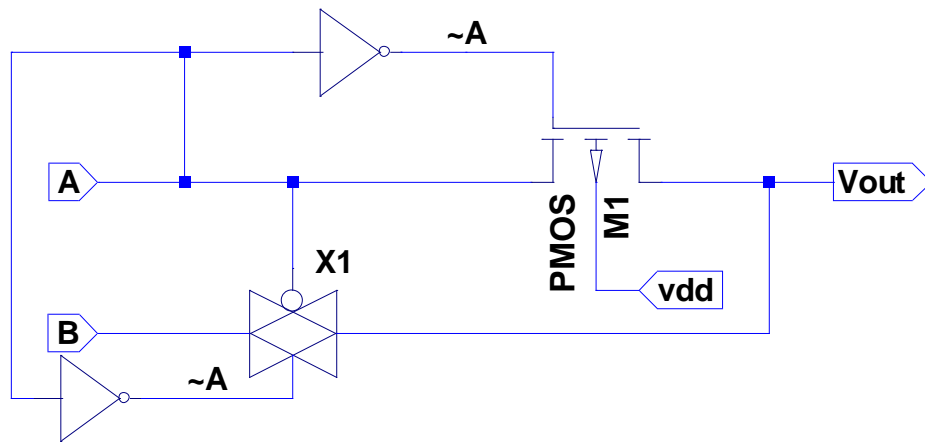


Figure 2: TG-based OR gate in LTSpice

 


Figure 3: OR gate symbol in LTSpice

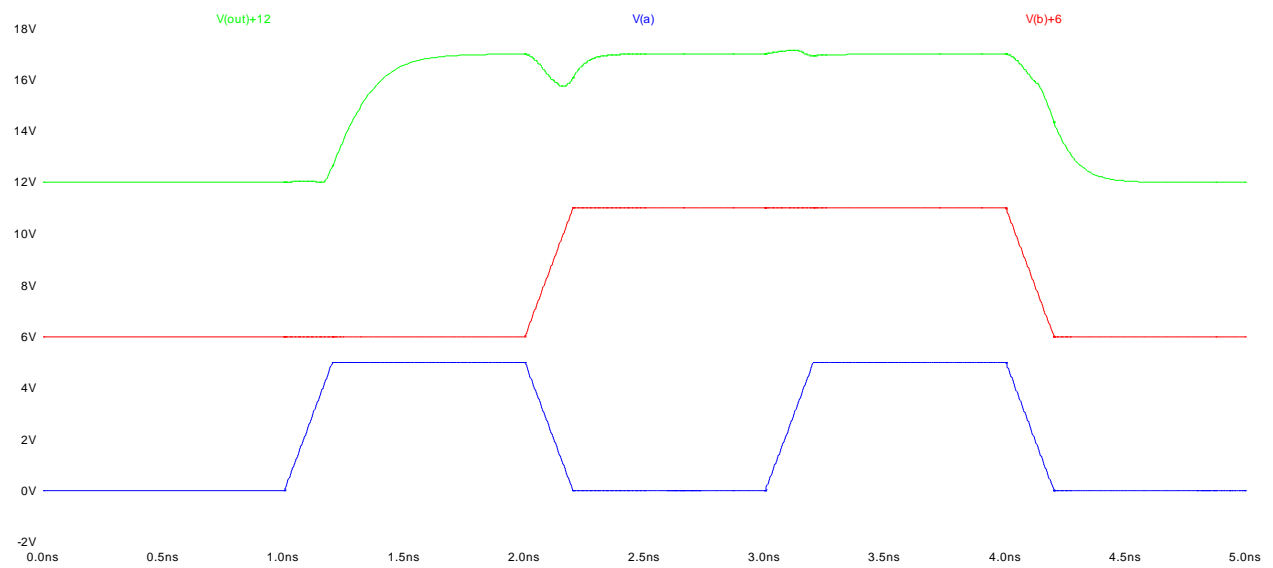


Figure 4: Output waveform of the test circuit

 


Figure 5: Output waveform for increased time period

From the above waveform, the green waveform represents the output of the OR gate. It is clear that when either of the inputs is high, the output is also high.

Hence verified.

Problem 2:

Cmos_nor

```
module cmos_nor(out,a,b);

parameter dly = 0;

input a,b;

output out;

wire w;

supply1 vdd;

supply0 vss;

nmos #dly m4(out,vss,b); // nmos 2

nmos #dly m3(out,vss,a); // nmos 1

pmos #dly m2(out,w,b); // pmos 2
```

```
pmos #dly m1(w,vdd,a);      // pmos 1
```

```
endmodule
```

nor_test

```
module nor_test;
```

```
reg a, b;
```

```
wire out,test;
```

```
cmos_nor g1(out,a,b);
```

```
assign test = ~(a|b);
```

```
initial
```

```
begin
```

```
    a = 1'b0; b = 1'b0;
```

```
#10
```

```
    a = 1'b0; b = 1'b1;
```

```
#10
```

```
    a = 1'b1; b = 1'b0;
```

```
#10
```

```
    a = 1'b1; b = 1'b1;
```

#10

```
a = 1'b0; b = 1'b0;
```

```
end
```

```
initial
```

```
$monitor("time %d a %b b %b out %b test %b %s",
```

```
$time,a,b,out,test,out==test? "valid":"invalid");
```

```
endmodule
```

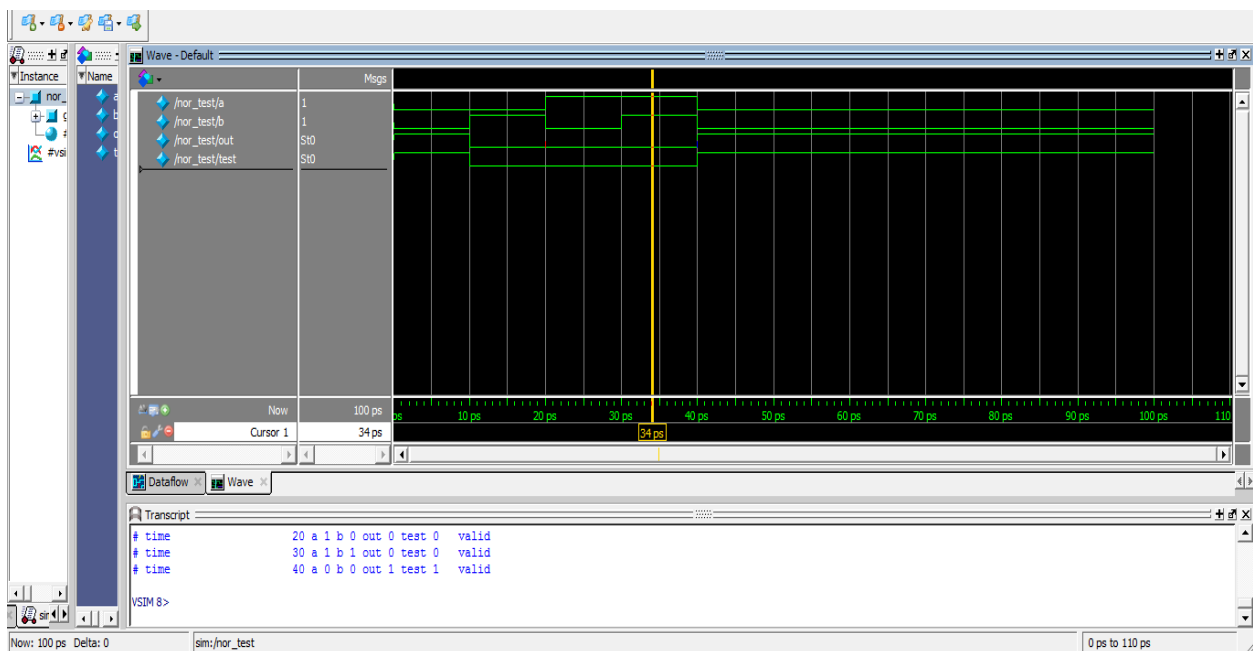


Figure 6: ModelSim output waveform of the NOR gate

ModelSim transcript window

```
add wave sim:/nor_test/*
VSIM 7> run
# time          0 a 0 b 0 out 1 test 1  valid
# time          10 a 0 b 1 out 0 test 0  valid
# time          20 a 1 b 0 out 0 test 0  valid
# time          30 a 1 b 1 out 0 test 0  valid
# time          40 a 0 b 0 out 1 test 1  valid
VSIM 8>]
```

Figure 7: ModelSim transcript window

Problem 3:

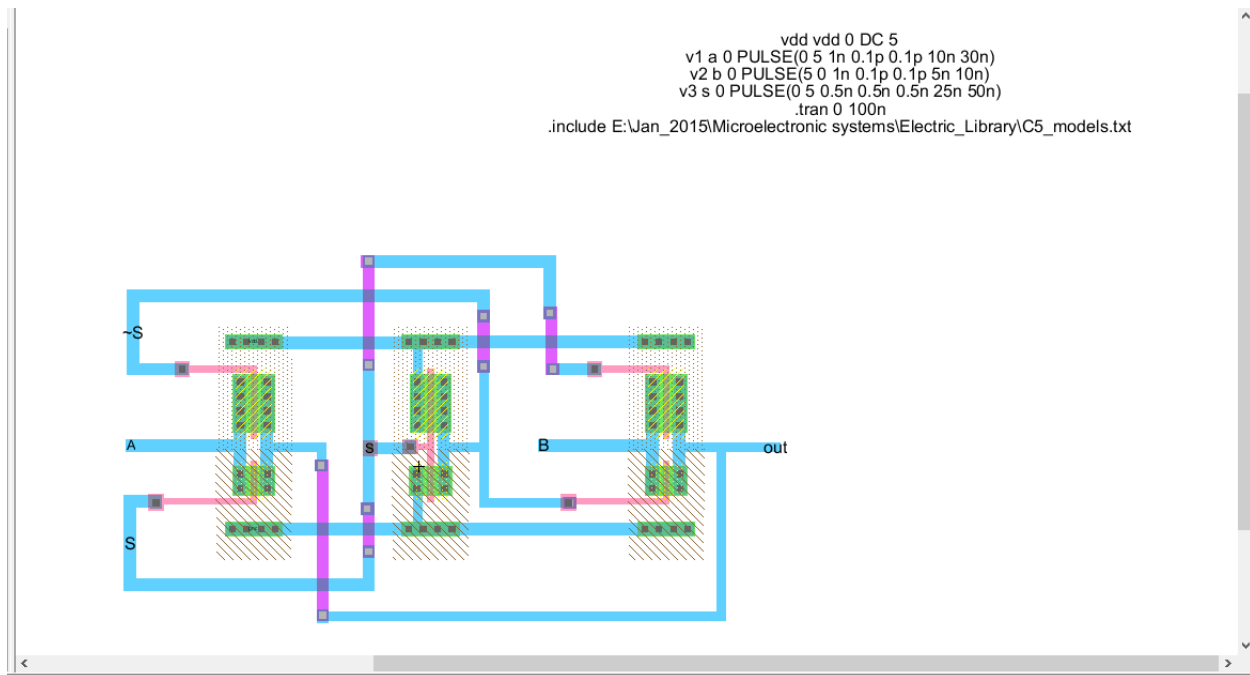


Figure 8: Layout of a multiplexer in Electric

```

mux_1.spi  mux_1.spi
*** SPICE deck for cell mux_1{lay} from library tutorial_5
*** Created on Thu Jan 07, 2010 20:19:07
*** Last revised on Fri Apr 03, 2015 15:38:03
*** Written on Fri Apr 03, 2015 19:51:52 by Electric VLSI Design System,
*** version 9.05
*** Layout tech: mcmos, foundry MOSIS
*** UC SPICE *** , MIN_RESIST 4.0, MIN_CAPAC 0.1FF

*** SUBCIRCUIT tutorial_5_inv_20_10 FROM CELL inv_20_10{lay}
.SUBCKT tutorial_5_inv_20_10 gnd in out vdd
Mnm0s00 out in gnd gnd NMOS L=0.6U W=3U AS=14.67P AD=8.415P PS=24.78U
+PD=12.75U
Mpm0s00 vdd in out vdd PMOS L=0.6U W=6U AS=8.415P AD=20.16P PS=12.75U
+PD=30.72U
.ENDS tutorial_5_inv_20_10

*** SUBCIRCUIT tutorial_5_transmission_gate FROM CELL transmission_gate{lay}
.SUBCKT tutorial_5_transmission_gate A gnd in out vdd _A
Mnm0s00 out A in gnd NMOS L=0.6U W=3U AS=8.415P AD=8.415P PS=12.75U PD=12.75U
Mpm0s00 in _A out vdd PMOS L=0.6U W=6U AS=8.415P AD=8.415P PS=12.75U
+PD=12.75U
.ENDS tutorial_5_transmission_gate

*** TOP LEVEL CELL: mux_1{lay}
Xinv_20_101 gnd S _S vdd tutorial_5_inv_20_10
Xtransmis00 S gnd A out vdd _S tutorial_5_transmission_gate
Xtransmis01 _S gnd B out vdd _S tutorial_5_transmission_gate

* Spice Code nodes in cell cell 'mux_1{lay}'
vdd vdd 0 DC 5
v1 a 0 PULSE(0 5 1n 0.1p 0.1p 10n 30n)
v2 b 0 PULSE(5 0 1n 0.1p 0.1p 5n 10n)
v3 s 0 PULSE(0 5 0.5n 0.5n 0.5n 25n 50n)
.tran 0 100n
.include E:\Jan_2015\Microelectronic systems\Electric_Library\C5_models.txt
.END

```

Figure 9: Spice netlist of the multiplexer layout

Output waveform

 


Figure 10: LTSpice output waveform

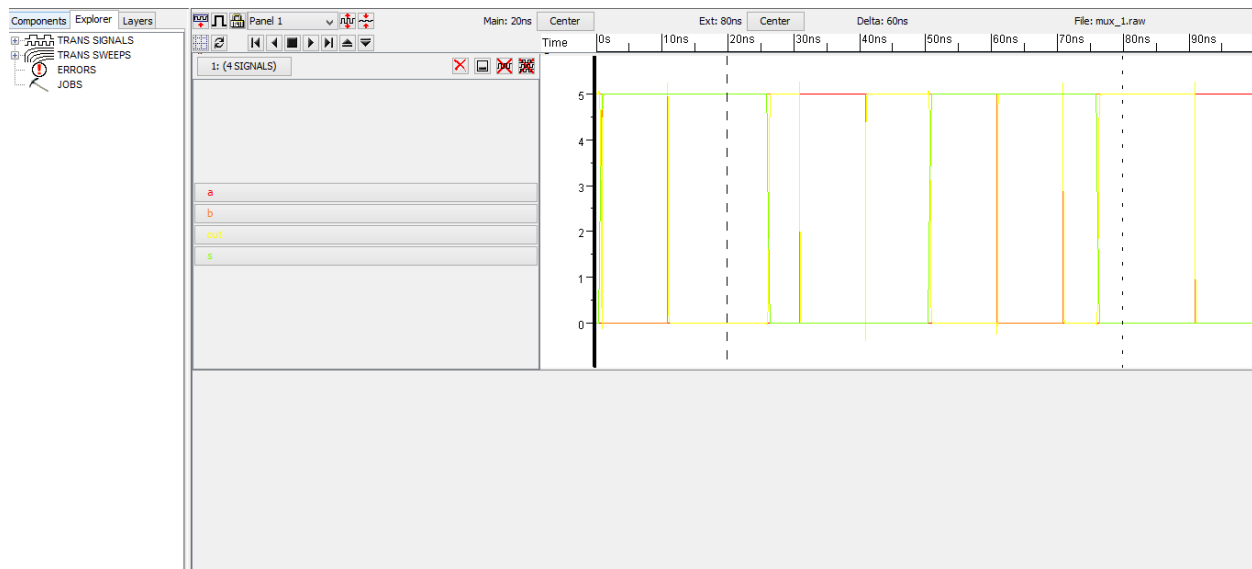


Figure 11: Multiplexer electric output

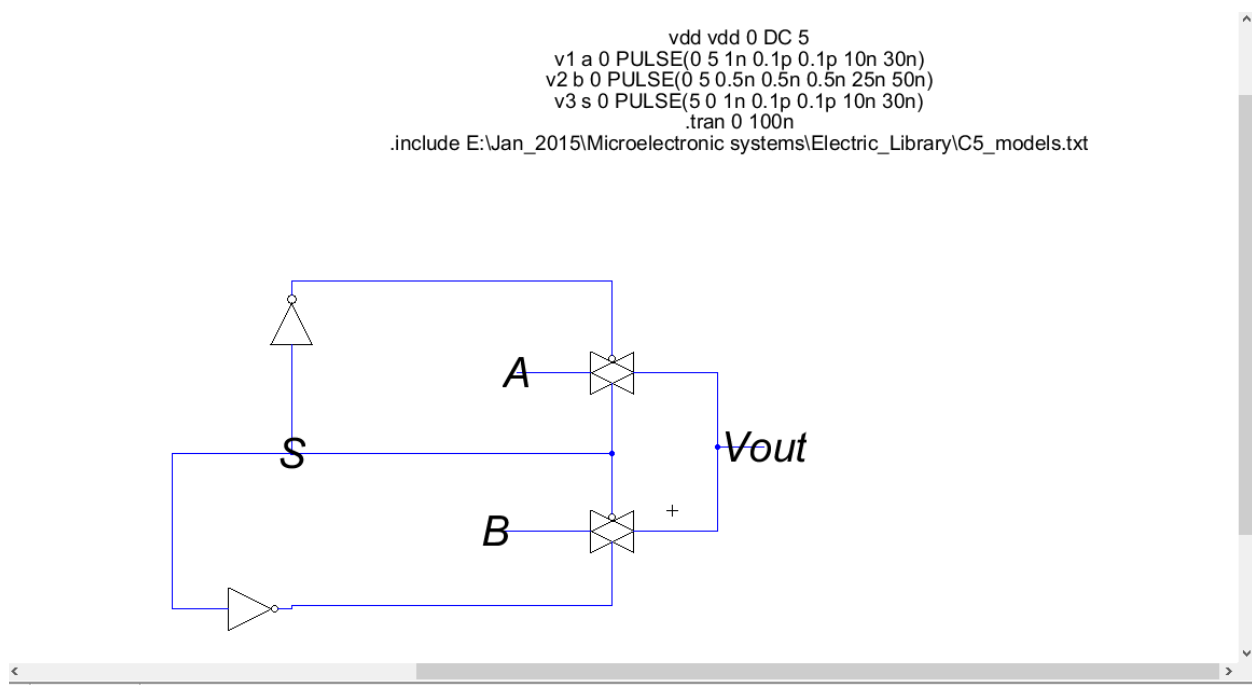


Figure 12: Schematic figure of multiplexer

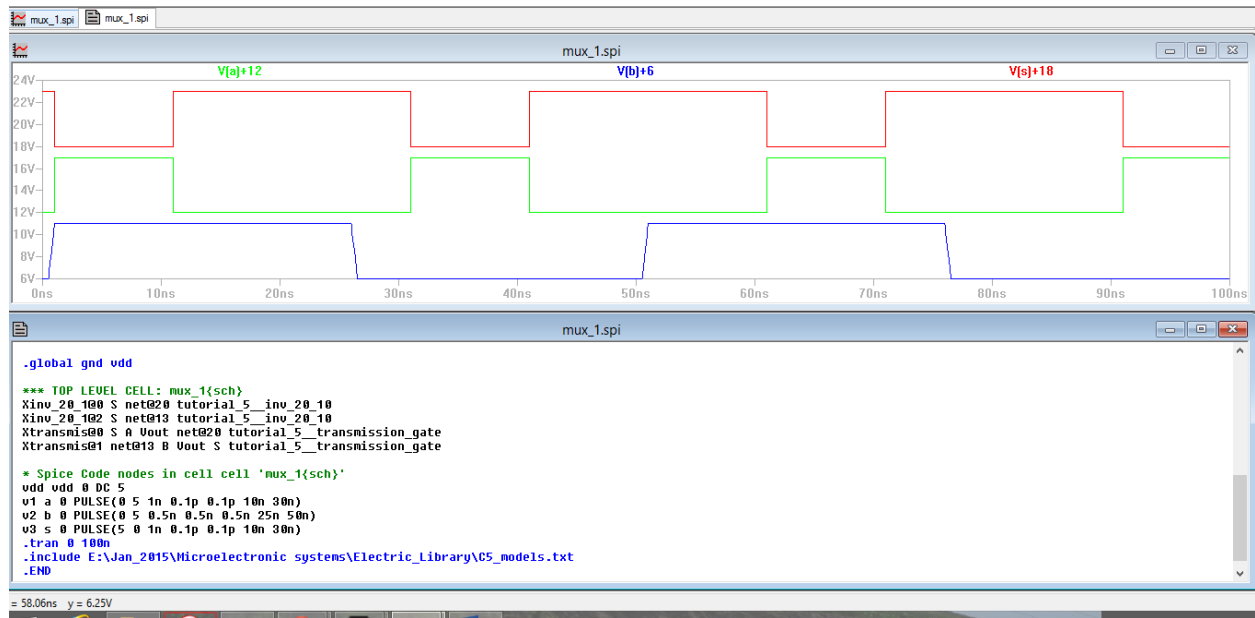


Figure 13: LTSpice simulation of the multiplier schematic

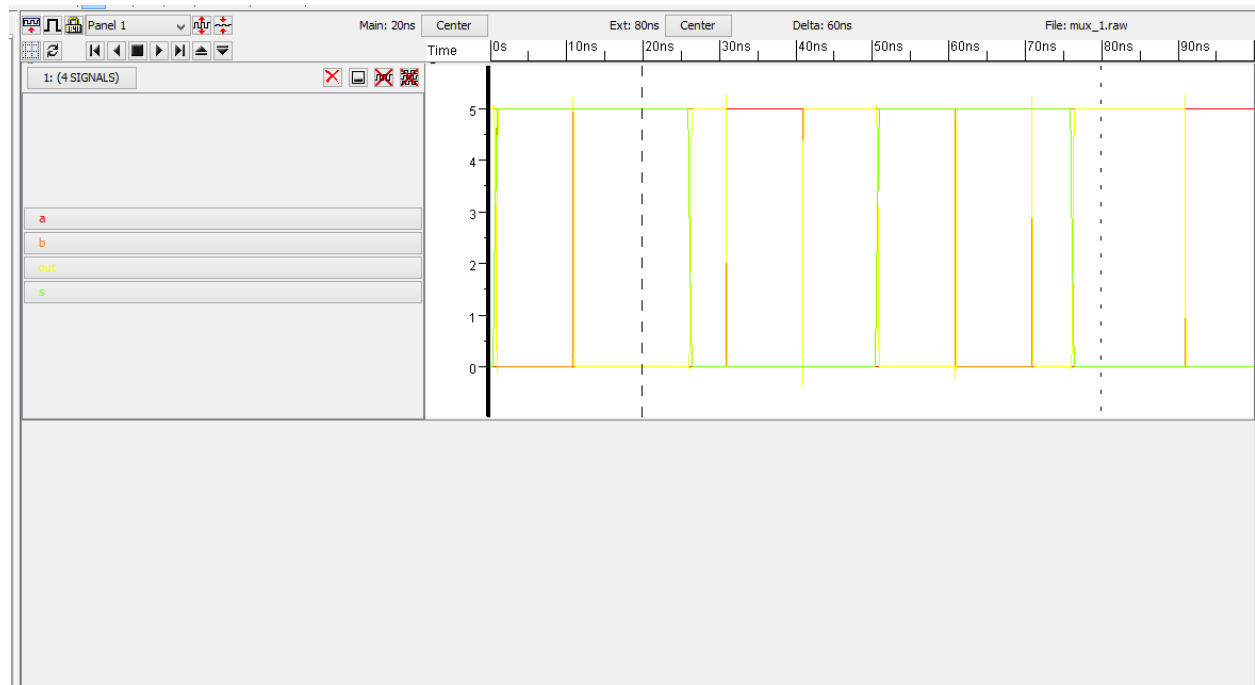


Figure 14: Electric simulation of the multiplexer

Test circuit in LTSpice

LTSpice test circuit:

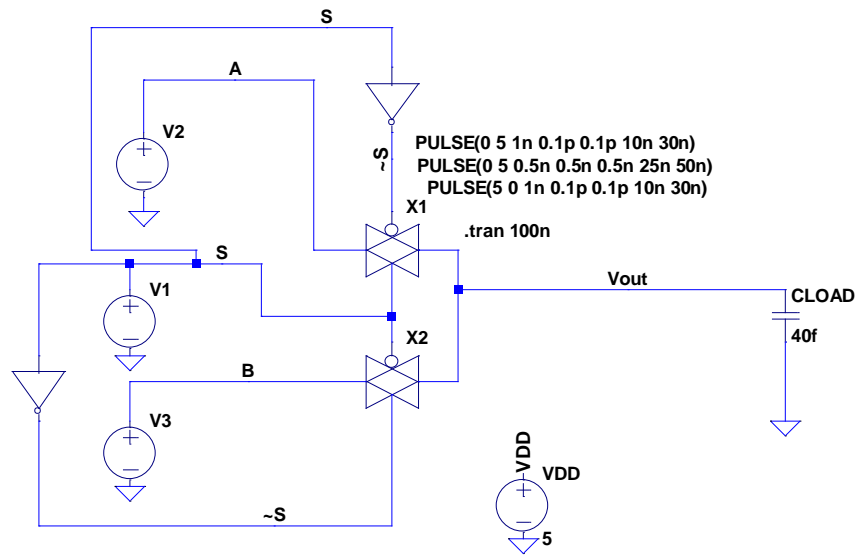


Figure 15: LTSpice circuit diagram of the multiplexer

 


Figure 16: LTSpice test circuit simulation of the multiplexer

Hence proved

Problem 4:

Layout of the transmission gate

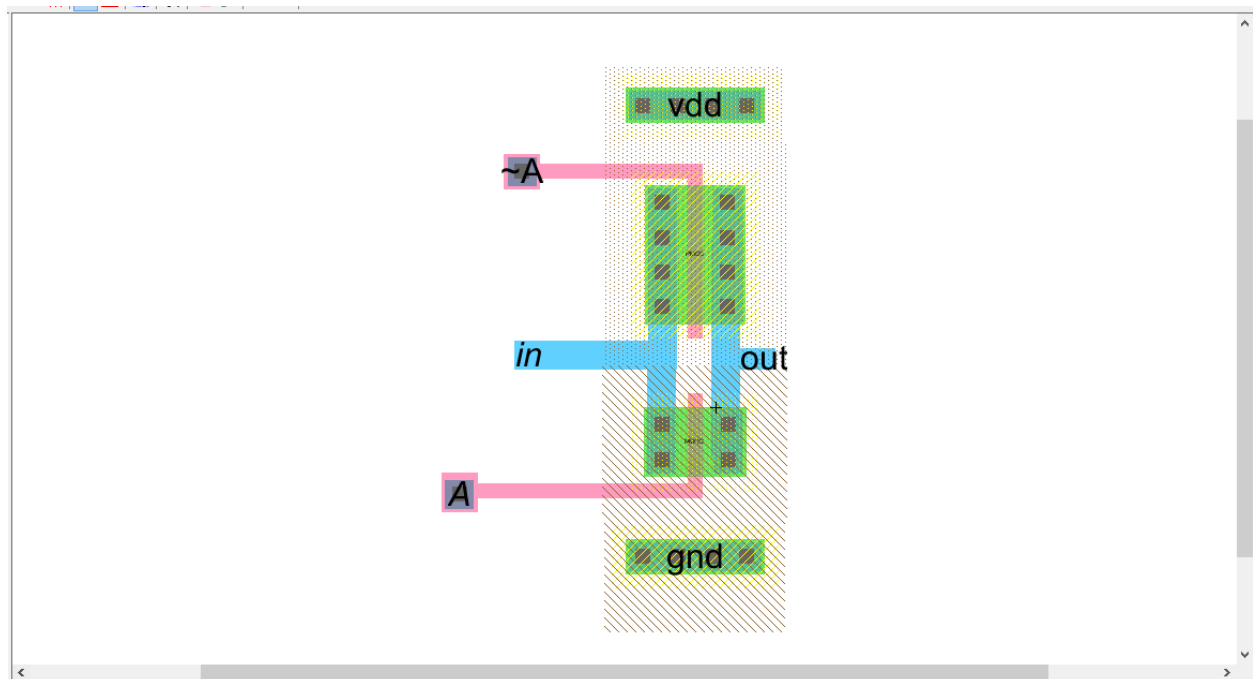


Figure 17: Layout of the transmission gate

 


Figure 18: Transmission gate icon

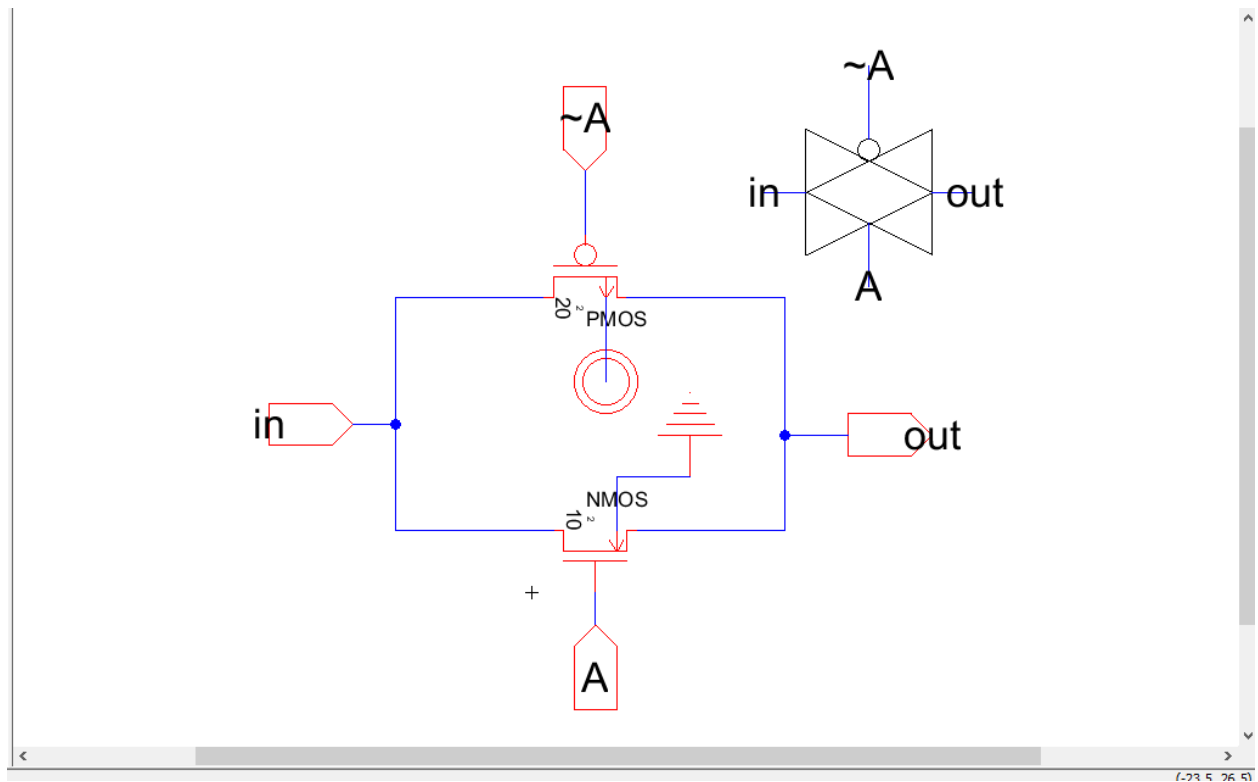


Figure 19: Transmission gate schematic

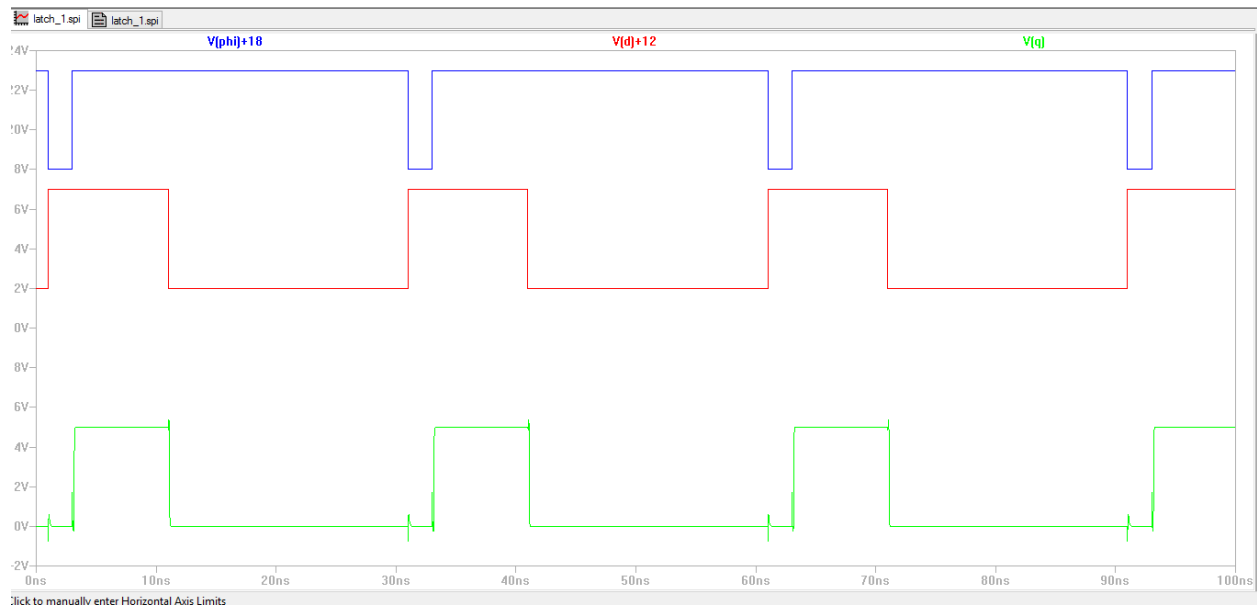


Figure 19: LTSpice simulation of the latch

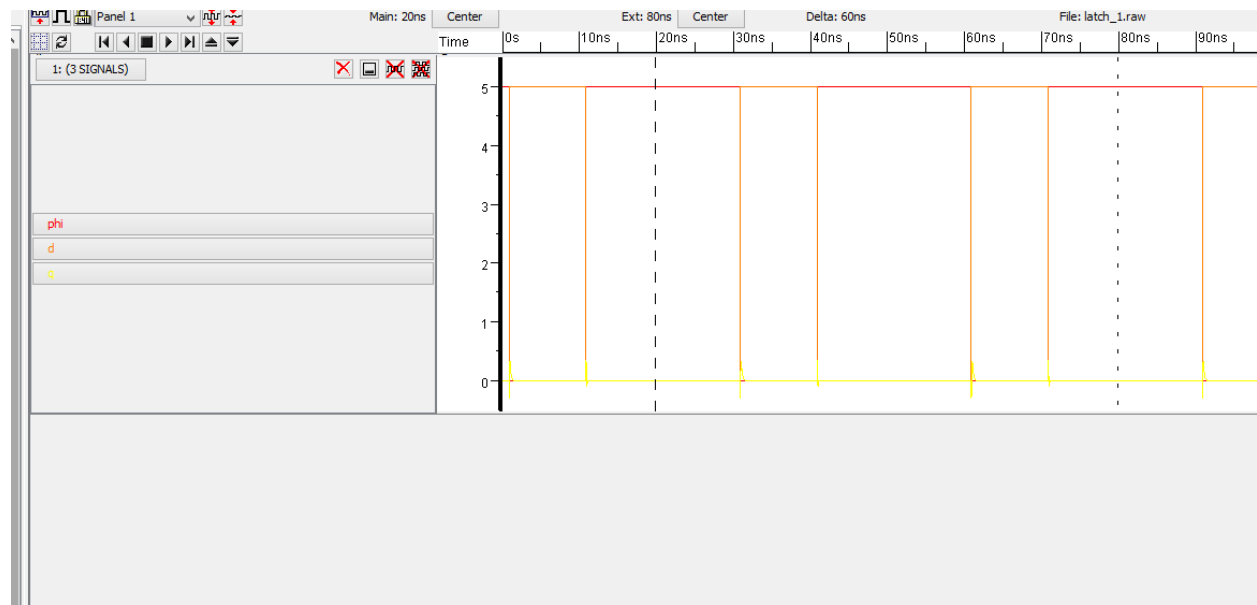


Figure 20: Electric simulation of the Latch

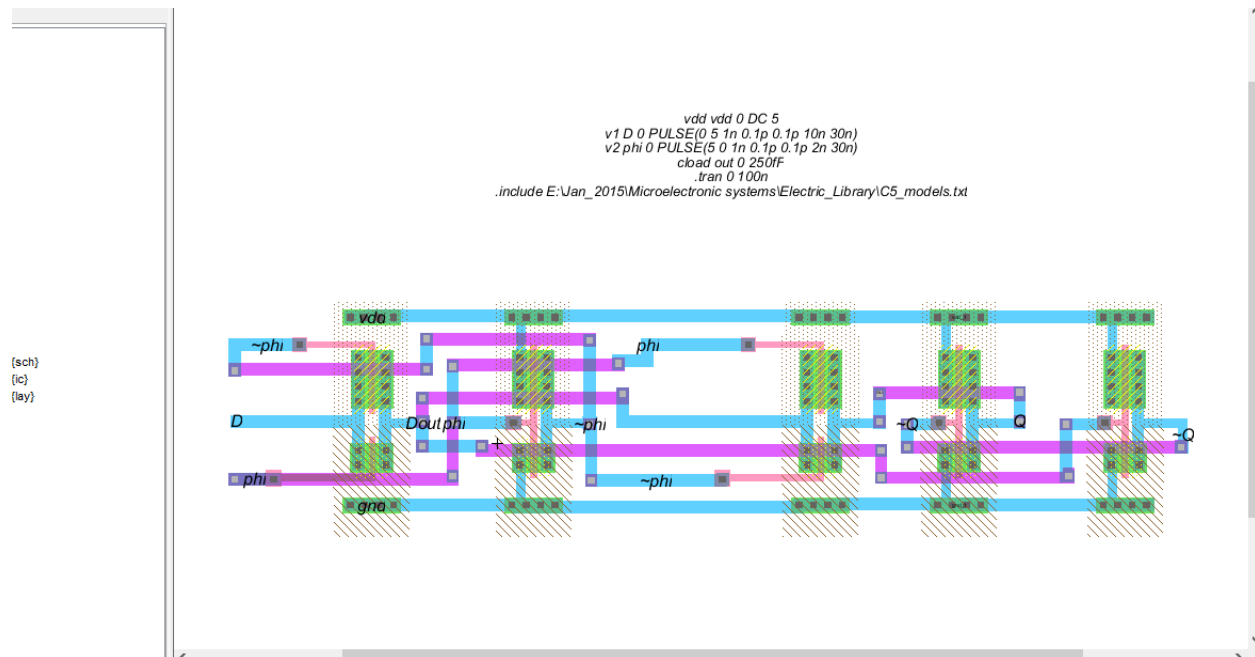


Figure 21: Layout of the Latch circuit

```

latch_1.spi  latch_1.spi
*** SPICE deck for cell latch_1{lay} from library tutorial_5
*** Created on Thu Jan 07, 2010 20:19:07
*** Last revised on Fri Apr 03, 2015 15:34:27
*** Written on Fri Apr 03, 2015 20:01:58 by Electric ULSI Design System,
*** version 9.05
*** Layout tech: mcmos, Foundry MOSIS
*** UC SPICE *** , MIN_RESIST 4.0, MIN_CAPAC 0.1FF

*** SUBCIRCUIT tutorial_5_inv_20_10 FROM CELL inv_20_10{lay}
.SUBCKT tutorial_5_inv_20_10 gnd in out vdd
Mnmos@0 out in gnd gnd NMOS L=0.6U W=3U AS=14.67P AD=8.415P PS=24.78U
+PD=12.75U
Mpmos@0 vdd in out vdd PMOS L=0.6U W=6U AS=8.415P AD=20.16P PS=12.75U
+PD=30.72U
.ENDS tutorial_5_inv_20_10

*** SUBCIRCUIT tutorial_5_transmission_gate FROM CELL transmission_gate{lay}
.SUBCKT tutorial_5_transmission_gate A gnd in out vdd _A
Mnmos@0 out A in gnd NMOS L=0.6U W=3U AS=8.415P AD=8.415P PS=12.75U PD=12.75U
Mpmos@0 in _A out vdd PMOS L=0.6U W=6U AS=8.415P AD=8.415P PS=12.75U
+PD=12.75U
.ENDS tutorial_5_transmission_gate

*** TOP LEVEL CELL: latch_1{lay}
Xinv_20_10@1 gnd phi _phi vdd tutorial_5_inv_20_10
Xinv_20_10@2 gnd _Q Q vdd tutorial_5_inv_20_10
Xinv_20_10@3 gnd Dout _Q vdd tutorial_5_inv_20_10
Xtransmis@0 phi gnd D Dout vdd _phi tutorial_5_transmission_gate
Xtransmis@1 _phi gnd Dout Q vdd phi tutorial_5_transmission_gate

* Spice Code nodes in cell cell 'latch_1{lay}'
vdd vdd 0 DC 5
v1 D 0 PULSE(0 5 1n 0.1p 0.1p 10n 30n)
v2 phi 0 PULSE(5 0 1n 0.1p 0.1p 2n 30n)
cload out 0 250fF
.tran 0 100n
.include E:\Jan_2015\Microelectronic systems\Electric_Library\C5_models.txt
.END

```

Figure 22: LTSpice netlist of the latch circuit

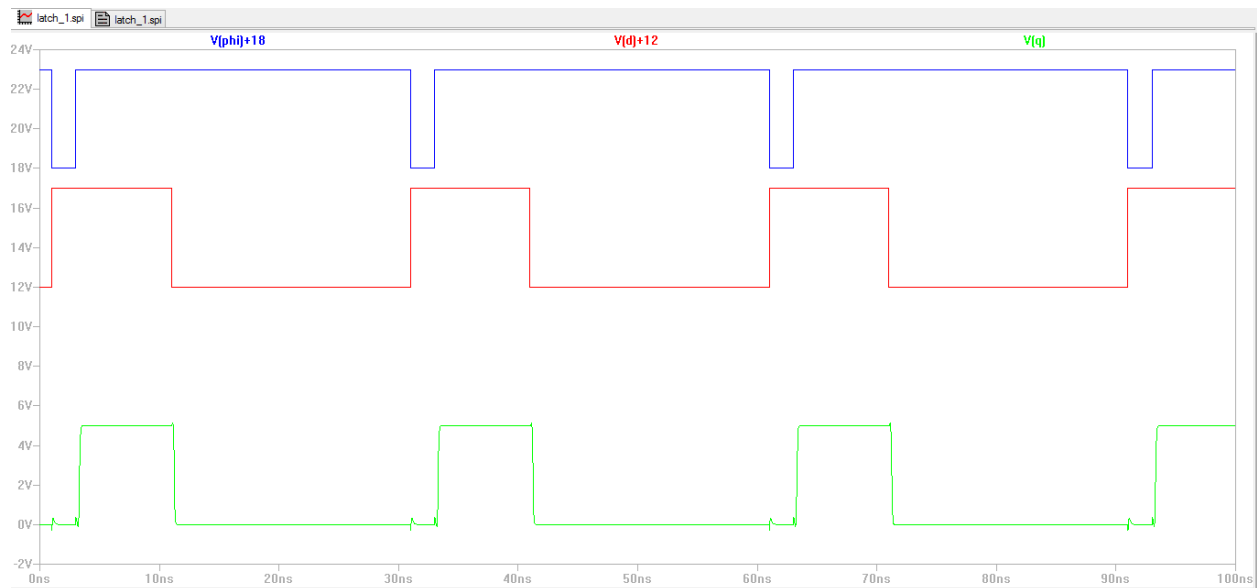


Figure 23: LTSpice simulation of the latch

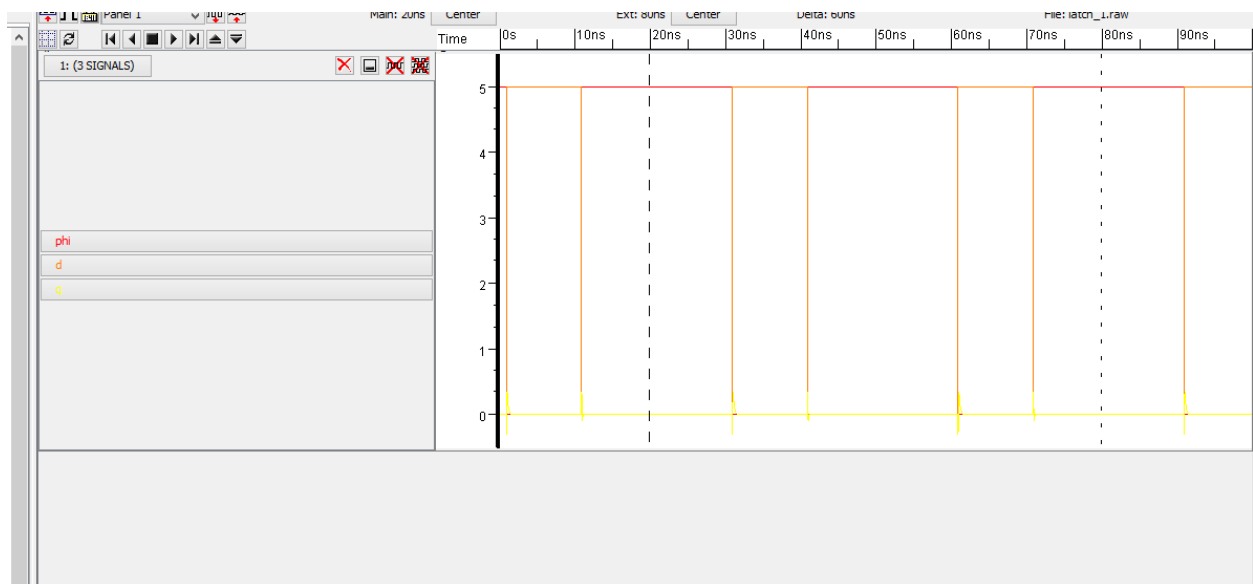


Figure 24: Electric simulation of the latch layout circuit

Test circuit of the Latch in LTSpice

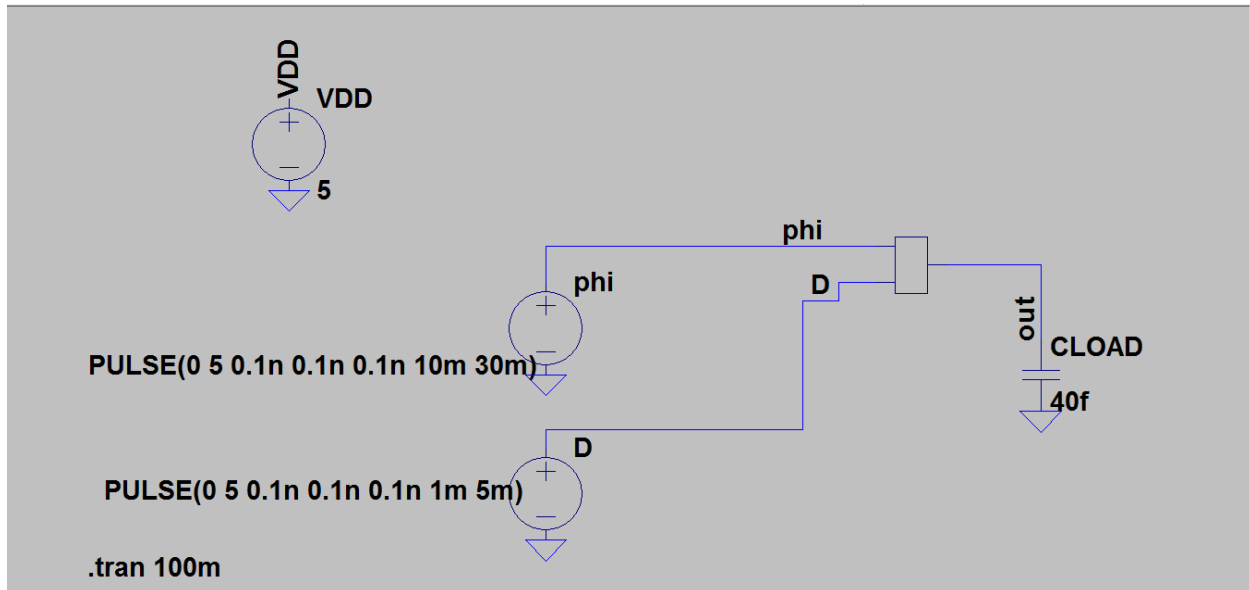


Figure 25: LTSPICE test circuit of the latch

 


Figure 26: Latch circuit in LTSpice

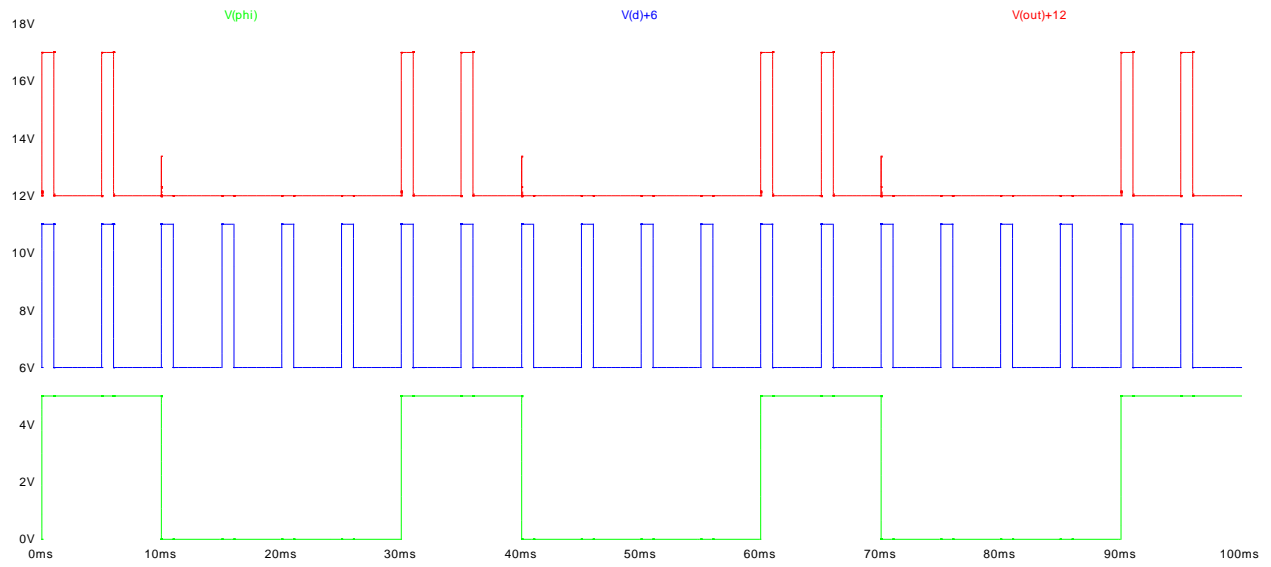


Figure 27: LTSPice simulation of the Latch test circuit